
BIRLA INSTITUTE OF TECHNOLOGY & SCIENCE, PILANI K. K. BIRLA Goa Campus

First Semester 2014-2015

CS F342 Computer Organization and Architecture Lab – 1, 14th August 2014

 Design and implement the following using verilog HDL in **ModelSim software** with the following specifications.



Modules

```
1.module D ff(input clk, input reset, input regWrite, input decOut1b, input d, output reg q);
     always @ (negedge clk)
     begin
     if(reset==1)
           q=0;
     else
           if(regWrite == 1 && decOut1b==1)
           begin
                 q=d;
           end
     end
endmodule
2.module register32bit(input clk, input reset, input regWrite, input decOut1b, input [31:0] writeData,
output [31:0] outR);
3. module registerSet(input clk, input reset, input regWrite, input [7:0] decOut, input [31:0] writeData,
output [31:0] outR0,outR1,outR2,outR3,outR4,outR5,outR6,outR7);
4. module decoder(input [2:0] destReg, output reg [7:0] decOut);
5. module mux8to1(input [31:0] outR0,outR1,outR2,outR3,outR4,outR5,outR6,outR7,
      input [2:0] Sel, output reg [31:0] outBus );
6. module registerFile(input clk, input reset, input regWrite, input [2:0] srcRegA, input [2:0] srcRegB,
     input [2:0] destReg, input [31:0] writeData, output [31:0] outBusA, output [31:0] outBusB);
```

```
7.module test_registerFile();
  //inputs
  reg clk,reset,regWrite;
  reg [2:0] srcRegA,srcRegB,destReg;
  reg [31:0] writeData;
  //outputs
  wire [31:0] outBusA;
  wire [31:0] outBusB;
  registerFile uut(clk,reset,regWrite,srcRegA,srcRegB,destReg,writeData,outBusA,outBusB);
  always begin #5 clk=~clk; end
  initial
  begin clk=0; reset=1; srcRegA=5'd0; srcRegB=5'd0;
  #5 reset=0; regWrite=1; destReg=3'd0; writeData=32'd8;
  #10 destReg=3'd1; writeData=32'd7;
  #10 destReg=3'd2; writeData=32'd6;
  #10 destReg=3'd3; writeData=32'd5;
  #10 destReg=3'd4; writeData=32'd4;
  #10 destReg=3'd5; writeData=32'd3;
  #10 destReg=3'd6; writeData=32'd2;
  #10 destReg=3'd7; writeData=32'd1;
  #10 regWrite=0; srcRegA=5'd7; srcRegB=5'd6;
  #10 srcRegA=5'd5; srcRegB=5'd4;
  #10 srcRegA=5'd3; srcRegB=5'd2;
  #10 srcRegA=5'd1; srcRegB=5'd0;
  #10 $finish;
  end
endmodule
```