

Design and implement Pipeline Implementation with following specifications.


**Instruction Format**


Instruction	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
	Opcode															
lw	0	0	rs			rt			Imm							
sw	0	1	rs			rt			Imm							
addi	1	0	rs			rt			Imm							
add	1	1	rs			rt			rd			X	X	X	X	0
sub	1	1	rs			rt			rd			X	X	X	X	1

**Control circuit**

Instruction	Opcode[15:14]	Opcode[0]	RegDst	ALUSrcB	ALUOp	MemRead	MemWrite	MemtoReg	RegWrite
lw	00	X	0	1	0	1	0	1	1
sw	01	X	X	1	0	0	1	X	0
addi	10	X	0	1	0	0	0	0	1
add	11	0	1	0	0	0	0	0	1
sub	11	1	1	0	1	0	0	0	1

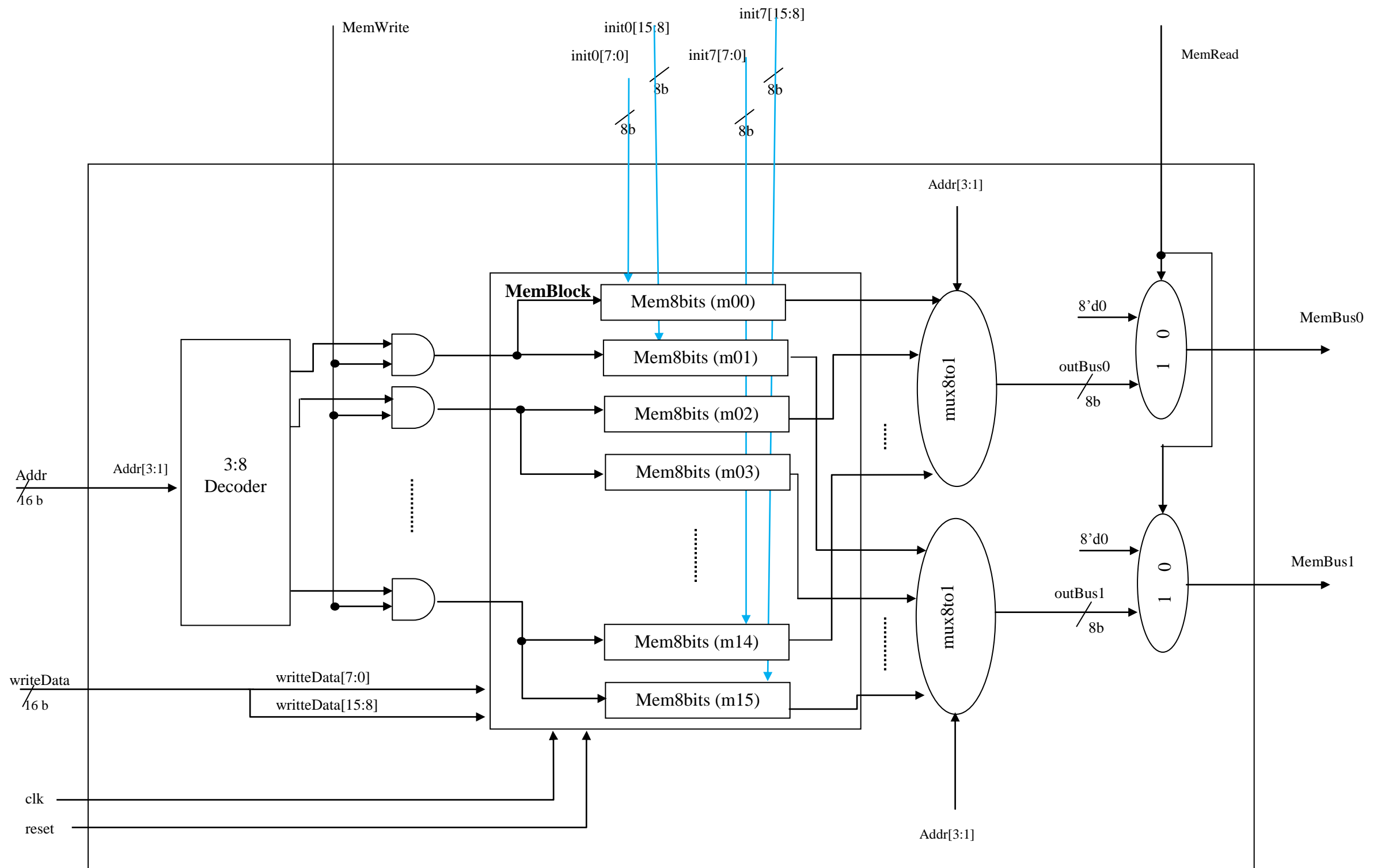1. module Memory(input clk, input reset, input [15:0] init0, init1, init2, init3, init4, init5, init6, init7, input MemWrite, input MemRead, input [15:0] Addr, input [15:0] writeData, output [7:0] MemBus0, output [7:0] MemBus1);
2. module Register16bit(input clk, input reset, input writeEn, input [15:0] writeData, output [15:0] outR);
3. module Register3bit(input clk, input reset, input writeEn, input [2:0] writeData, output [2:0] outR);
4. module Register1bit(input clk, input reset, input writeEn, input writeData, output outR);
5. module RegisterFile(input clk, input reset, input regWrite, input [2:0] srcRegA, input [2:0] srcRegB, input [2:0] destReg, input [15:0] writeData, output [15:0] outBusA, output [15:0] outBusB);
6. module IF\_ID\_PipelineRegister(input clk, input reset, input regWrite, input [15:0] instr, output [15:0] IR);
7. module ID\_EX\_PipelineRegister(input clk, input reset, input regWrite, input [15:0] BusA, input [15:0] BusB, input [15:0] SignExt8to16Imm, input [2:0] rd, input [2:0] rt, input ALUSrcB, input ALUOp, input RegDst, input MemRead, input MemWrite, input MemToReg, input RegWrite, output [15:0] P2BusA, output [15:0] P2BusB, output [15:0] P2SignExt8to16Imm, output [2:0] P2rd, output [2:0] P2rt, output P2ALUSrcB, output P2ALUOp, output P2RegDst, output P2MemRead, output P2MemWrite, output P2MemToReg, output P2RegWrite);
8. module EX\_MEM\_PipelineRegister(input clk, input reset, input regWrite, input [15:0] ALUOut, input [15:0] BusB, input [2:0] DstReg, input MemRead, input MemWrite, input MemToReg, input RegWrite, output [15:0] P3ALUOut, output [15:0] P3BusB, output [2:0] P3DstReg, output P3MemRead, output P3MemWrite, output P3MemToReg, output P3RegWrite);
9. module MEM\_WB\_PipelineRegister(input clk, input reset, input regWrite, input [15:0] ALUOut, input [15:0] DMOut, input [2:0] DstReg, input RegWrite, input MemToReg, output [15:0] P4ALUOut, output [15:0] P4DMOut, output [2:0] P4DstReg, output P4RegWrite, output P4MemToReg);
10. module ALU(input [15:0] in1, input [15:0] in2, input ALUOp, output reg [15:0] ALUOut);
11. module SignExt8to16(input [7:0] in, output reg [15:0] SignExtOut);
12. module Mux2to1\_16bits(input [15:0] in1, input [15:0] in2, input Sel, output reg [15:0] MuxOut);
13. module Mux2to1\_3bits(input [2:0] in1, input [2:0] in2, input Sel, output reg [2:0] MuxOut);
14. module CtrlCkt(input [1:0] opcode, input funcCode, output reg ALUSrcB, output reg ALUOp, output reg RegDst, output reg MemRead, output reg MemWrite, output reg MemToReg, output reg RegWrite);
15. module PCadder(input [15:0] in, output reg [15:0] out);
16. module TopModule(input clk, input reset, output [15:0] RegWriteData);



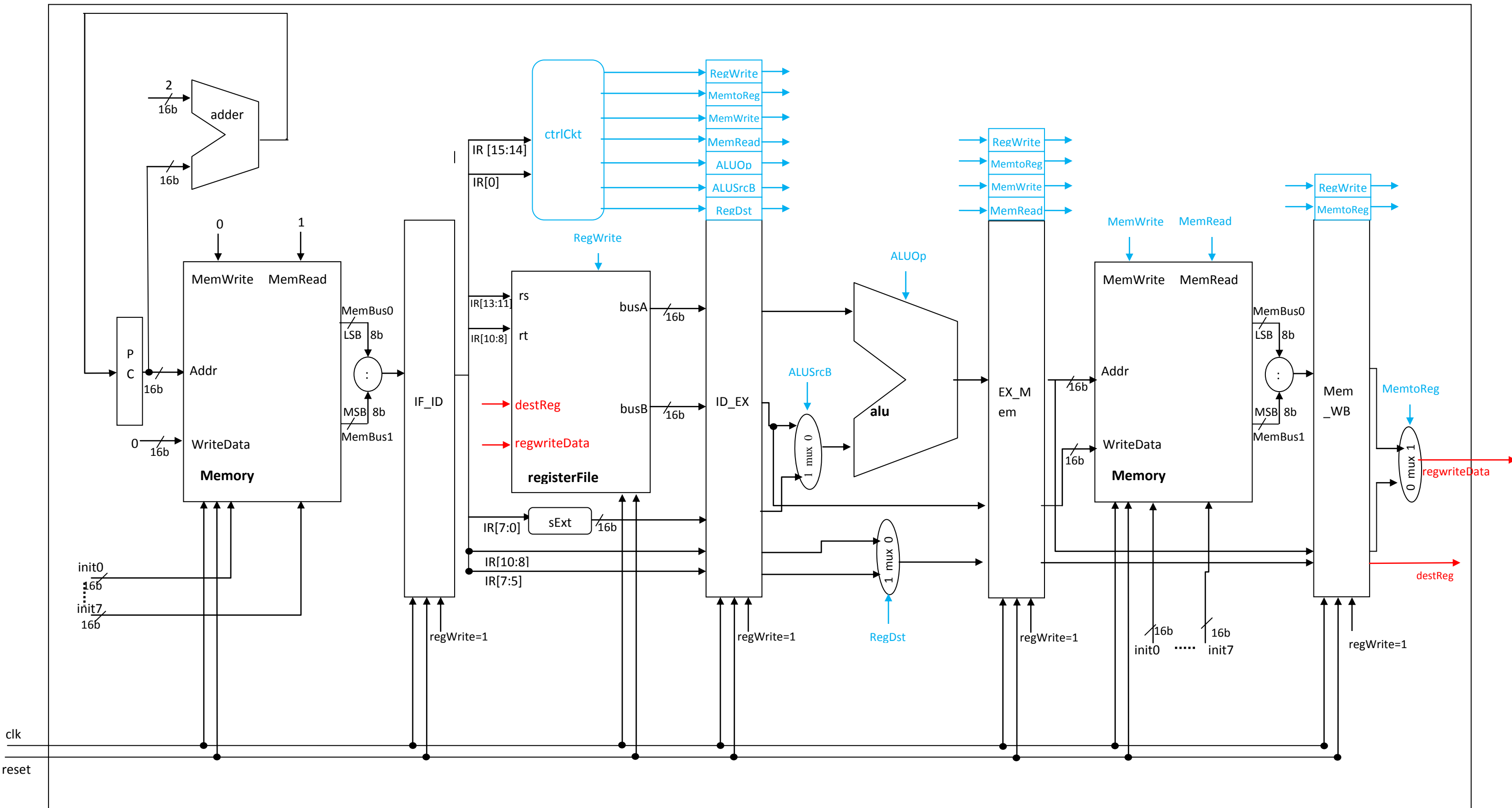

```

module testBench;
    reg clk, reset;
    wire [15:0] RegWriteData;
    TopModule uut (.clk(clk), .reset(reset), .RegWriteData(RegWriteData));
    always
        #5 clk=~clk;
    initial
    begin
        clk = 0; reset = 1;
        #10 reset=0;
        #130 $finish;
    end
endmodule

```

